

Expt. 2 IC 555 and ADC (0804)

Aim: To Understand the working of

the IC 555 and ADC



Used for
generating
CLOCK
(Square wave)



for converting
voltages to
digital values
(binary)

555 Timer

- a very popular integrated Circuit (IC) for Timer applications → as a multivibrator

- Multivibrator vs Oscillator




one that gives
Square wave output
(or rectangular)




Sinusoidal o/p

- Astable Multivibrator → Continuous square wave/rectangular
- Monostable Multivibrator → produces ONE pulse when triggered (ONE stable state)
- Bistable Multivibrator → Two stable states
-(when triggered toggles between the two)

 555 Timer - equivalent Circuit for operations



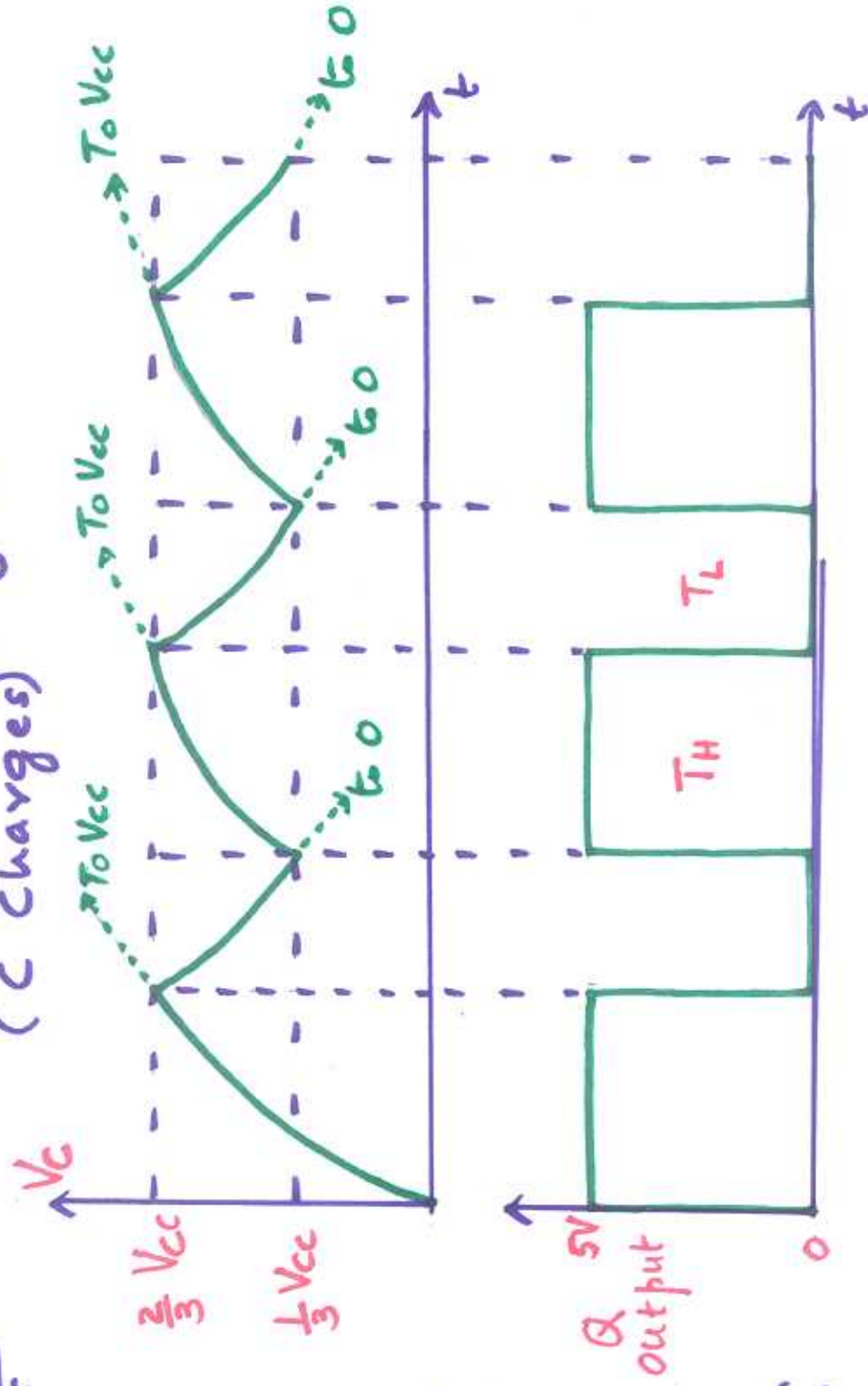- Switch S OPEN for $V_c \leq \frac{2}{3} V_{cc}$ (C charges)
- Switch S CLOSES for $V_c > \frac{2}{3} V_{cc}$ (C discharges) and S REMAINS CLOSED till $V_c > \frac{1}{3} V_{cc}$
- S OPENS when $V_c < \frac{1}{3} V_{cc}$ (C charges)




$$T_H = 0.69 (R_A + R_B) \cdot C$$

$$T_L = 0.69 R_B \cdot C$$

$$f = \frac{1}{T}, T = T_H + T_L$$

$$T = 0.69 (R_A + 2R_B) \cdot C$$

555 Timer Block Diagram

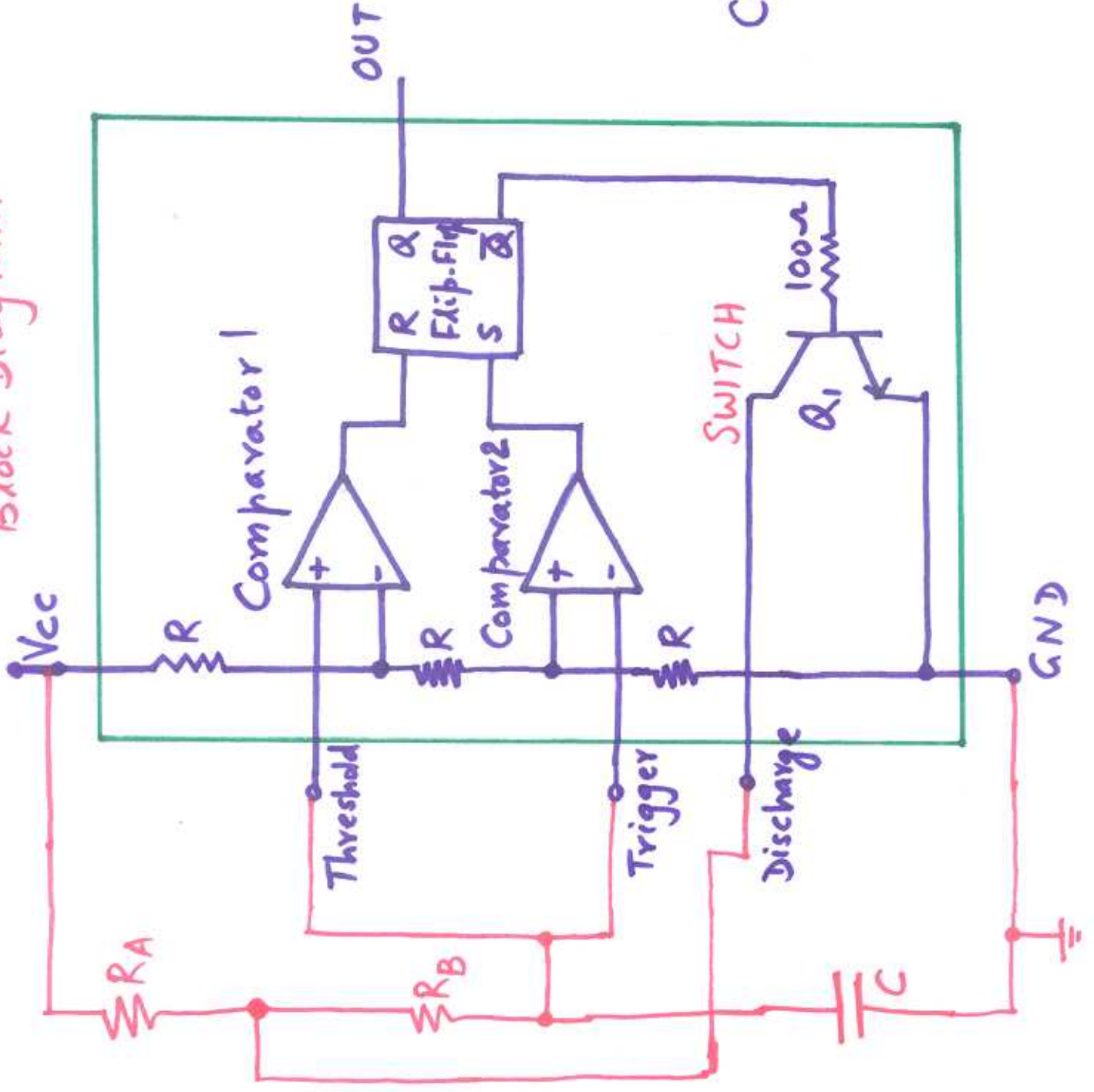


RS Flip-Flop

R	S	Q	\bar{Q}	
1	0	0	1	Reset
0	0	0	1	Hold
0	1	1	0	Set
0	0	1	0	Hold
1	1	Not allowed		

Comparator output



HIGH if $V_+ > V_-$

LOW if $V_+ < V_-$

 



V_c	Compa- rator 1 (=R)	Compa- rator 2 (=S)	MODE	Q	\bar{Q}	SWITCH	Action
$< \frac{1}{3} V_{cc}$	0	1	SET	1	0	OPEN	C Charging
$\frac{1}{3} V_{cc} < V_c < \frac{2}{3} V_{cc}$	0	0	HOLD	1	0	OPEN	C Charging
$> \frac{2}{3} V_{cc}$	1	0	RESET	0	1	CLOSED	C Discharging
$\frac{1}{3} V_{cc} < V_c < \frac{2}{3} V_{cc}$	0	0	HOLD	0	1	CLOSED	C Discharging
$< \frac{1}{3} V_{cc}$	0	1	SET	1	0	OPEN	C Charging

  The "clock" signal is provided by a 555 timer circuit.



$$T = 0.7 (R_a + 2R_b) C$$

$$f = \frac{1}{T}$$

  

5V

VCC

Discharge

threshold

Control Voltage

ground-1

Trigger-2

output-3

reset-4

x

HIGH if 1
LOW if 0.

DB0

DB1

DB2-30V

DB4

DB5

DB6

DB7

5V

Analog to Digital Converter

Digital (binary) representation

567
↑ ↑ ↑
 5×10^2 6×10^1 7×10^0

$$101101 = 32 + 0 + 8 + 4 + 0 + 1$$

$$= 45 \text{ decimal}$$

$$\begin{array}{ccccccc} 1 & 0 & 1 & 1 & 0 & 1 & \\ \uparrow & & \uparrow & \uparrow & \uparrow & \uparrow & \uparrow \\ \times 2^5 & & \times 2^4 & \times 2^3 & \times 2^2 & \times 2^1 & \times 2^0 \end{array}$$

$$101101 \Big|_{\text{base 2}} = 45 \Big|_{\text{base 10}}$$

$N \text{ bits} \Rightarrow 2^N \text{ binary numbers}$


Analog to digital conversion

Why digital?


- * easier design
- * easy to store
- * things can be programmed!
- * less vulnerable to noise (see next page)
- * can integrate large number of functions
(on a chip)

Transmission: effect of noise / interference


Analog

 

Digital

 


Comparator

 

+5 if $V_+ > V_-$
0V if $V_+ < V_-$

 Can recover the original data by using a comparator.




Why digital?

1.357V \rightarrow 0101011.

* We may want to display a temperature



* Control application

 


- It is easy to implement control algorithms using DSP chips
- DSP chips can be re-programmed if we want to change the algorithm.

A to D examples

* Full scale measurement range: 0 to 10V

ADC resolution: 12 bits $\rightarrow 2^{12} = 4096$ quantization levels
 
$$\text{ADC voltage resolution} = \frac{10\text{V} - 0\text{V}}{4096} = 2.44 \text{ mV}$$



$$\text{LSB } 2^0 \rightarrow 0\text{V}$$

$$0000\ 0000\ 0000 \rightarrow 0\text{V}$$

$$0000\ 0000\ 0001 \rightarrow 2.44 \text{ mV}$$


MSB
 2^{11}

$$1111\ 1111\ 1111 \rightarrow 10\text{V} - 2.44 \text{ mV}$$

$$\left[= 10\text{V} \times \left(\frac{4095}{4096} \right) \right]$$

* Some ADCs allow negative voltages, e.g., -10V to +10V.

Digital transmission

 

Convert each "sample" from analog to digital.

Say, we have 8 bits to represent each signal sample.

Bandwidth = $8 \times$ sampling rate


MP3: 128 kbps, sampling rate = 44 kHz

~ 3 bits per sample ?!

This is allowed by compression algorithms

GSM: 13 kbps, $f_s = 8$ kHz


Digital-to-Analog Converter (DAC)

 

$$V_{out} = V_{REF} \left[1 \cdot S_3 + \frac{1}{2} \cdot S_2 + \frac{1}{4} \cdot S_1 + \frac{1}{8} \cdot S_0 \right]$$


S_3, S_2, S_1, S_0 take either '0' or '1'

S_3	S_2	S_1	S_0	Decimal Equivalent
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
				...
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

 


A Simple Analog-to-Digital Converter (ADC)

Counting-ADC

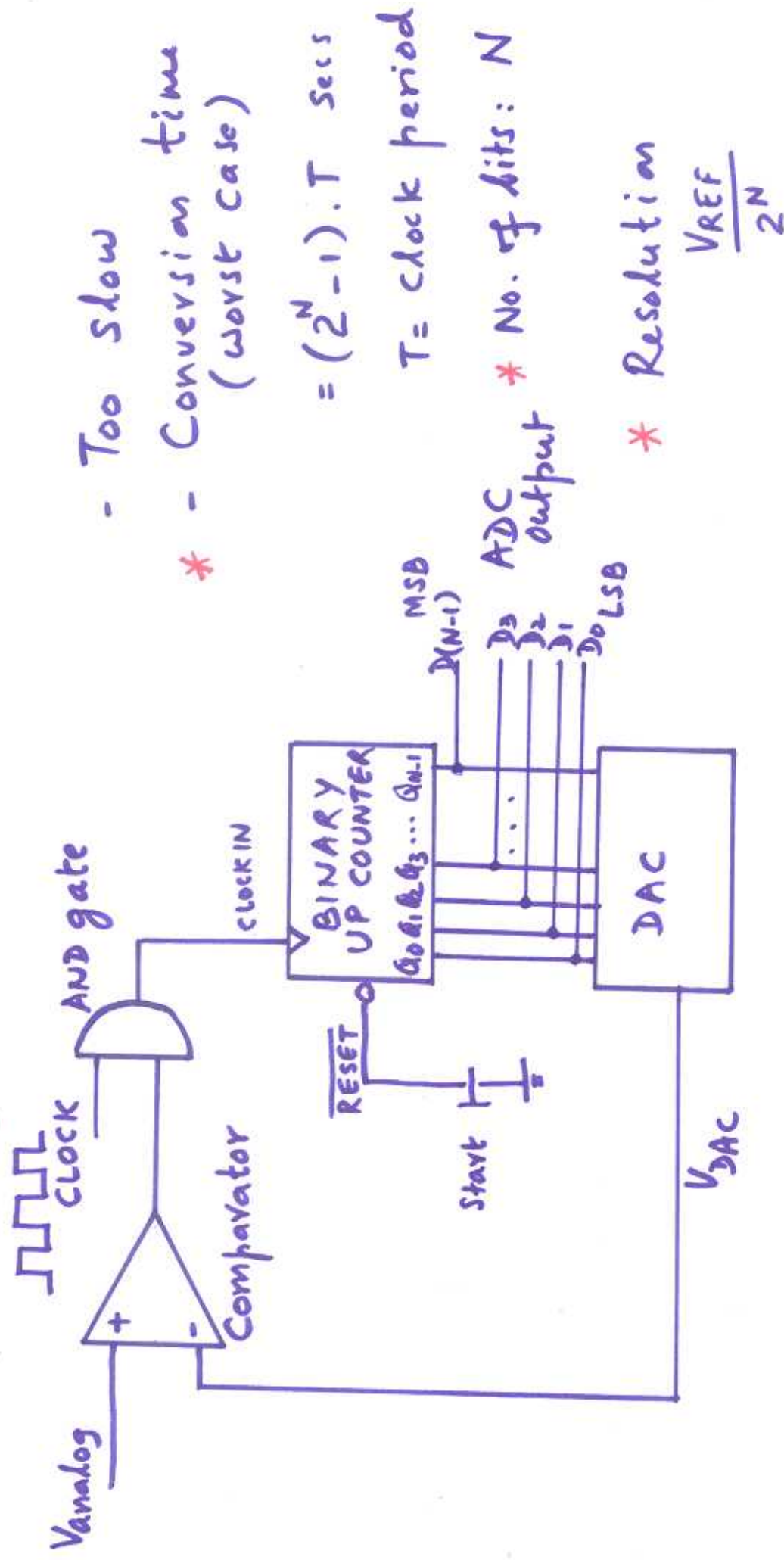

Successive approximation ADC


 


example

②	1111
③	1110
①	1101
	1100
	1011
	1010
	1001
	1000
	0111
	0110
	0101
	0100
	0011
	0010
	0001
	0000

V_{in}

Flash ADC

  


8-Bit, Microprocessor-Compatible, A/D Converters

The ADC080X family are CMOS 8-Bit, successive-approximation A/D converters which use a modified potentiometric ladder and are designed to operate with the 8080A control bus via three-state outputs. These converters appear to the processor as memory locations or I/O ports, and hence no interfacing logic is required.

The differential analog voltage input has good common-mode-rejection and permits offsetting the analog zero-input-voltage value. In addition, the voltage reference input can be adjusted to allow encoding any smaller analog voltage span to the full 8 bits of resolution.

Typical Application Schematic

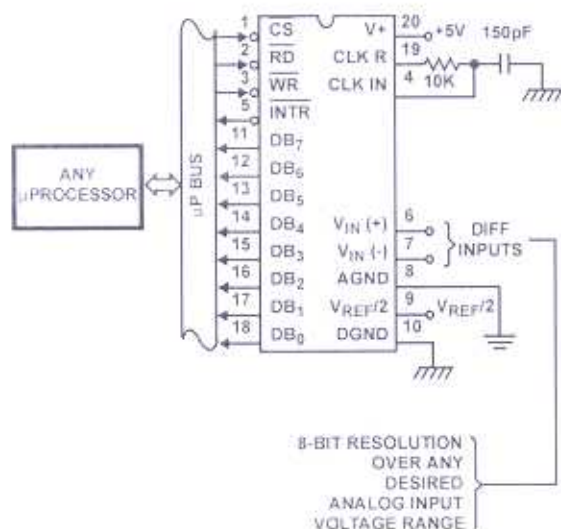


Features

- 80C48 and 80C80/85 Bus Compatible - No Interfacing Logic Required
- Conversion Time <100µs
- Easy Interface to Most Microprocessors
- Will Operate in a "Stand Alone" Mode
- Differential Analog Voltage Inputs
- Works with Bandgap Voltage References
- TTL Compatible Inputs and Outputs
- On-Chip Clock Generator
- Analog Voltage Input Range (Single +5V Supply) 0V to 5V
- No Zero-Adjust Required
- 80C48 and 80C80/85 Bus Compatible - No Interfacing Logic Required

Pinout

ADC0803, ADC0804 (PDIP)

TOP VIEW

 

Ordering Information

PART NUMBER	ERROR	EXTERNAL CONDITIONS	TEMP. RANGE (°C)	PACKAGE	PKG. NO.
ADC0803LCN	±1/2 LSB	VREF/2 Adjusted for Correct Full Scale Reading	0 to 70	20 Ld PDIP	E20.3
ADC0804LCN	±1 LSB	VREF/2 = 2.500V _{DC} (No Adjustments)	0 to 70	20 Ld PDIP	E20.3


 


FIGURE 10A. START CONVERSION

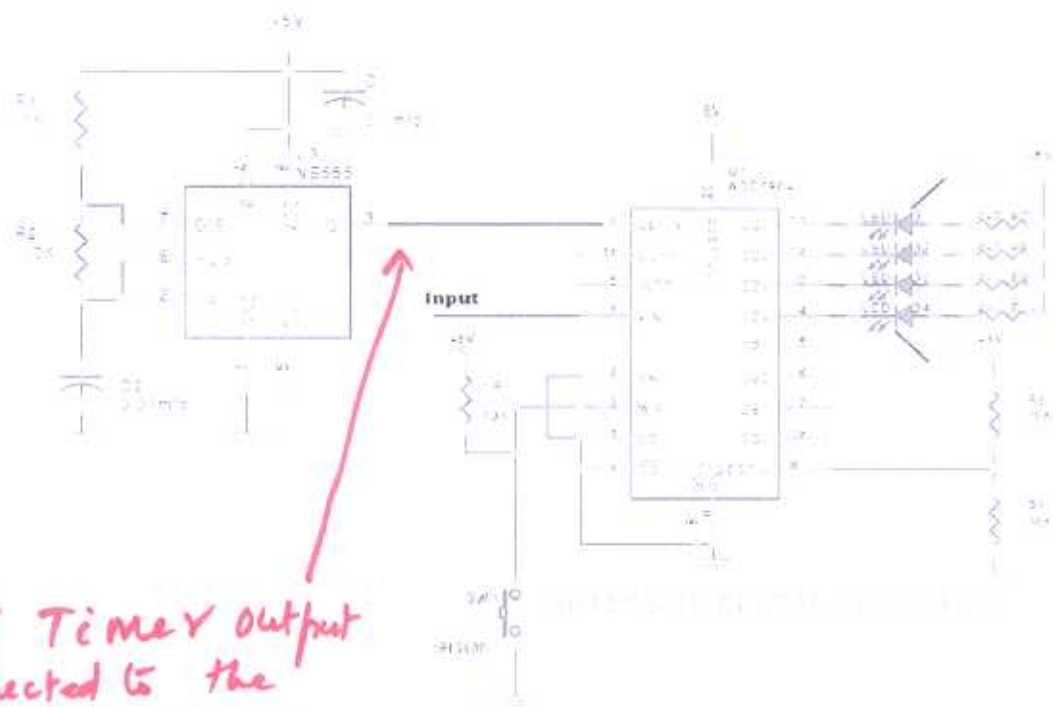

555 Timer output
connected to the
ADC CLOCK IN.

\overline{CS} - Chip select } connected to GND
 \overline{RD} - Read }
 \overline{WR} - write

ADC conversion initiated by
 pressing switch SW1 (making $\overline{WR} = '0'$)